

# Circuit Wizardry!

JCC Workshop #4






# Rules

You will be tested on all of the content covered in these slides, as well as some simple Ohm's Law calculations.

There may also be a lab portion similar to the labs we run today.




# Get a load of this

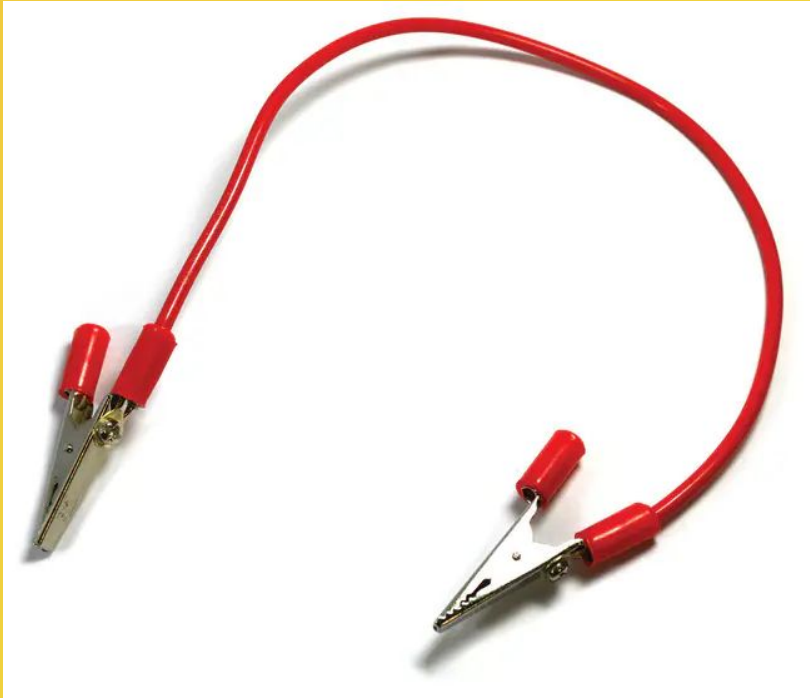

01

# What is a Circuit?

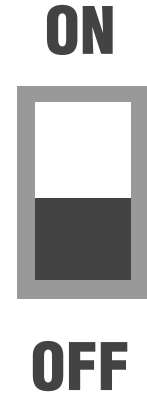



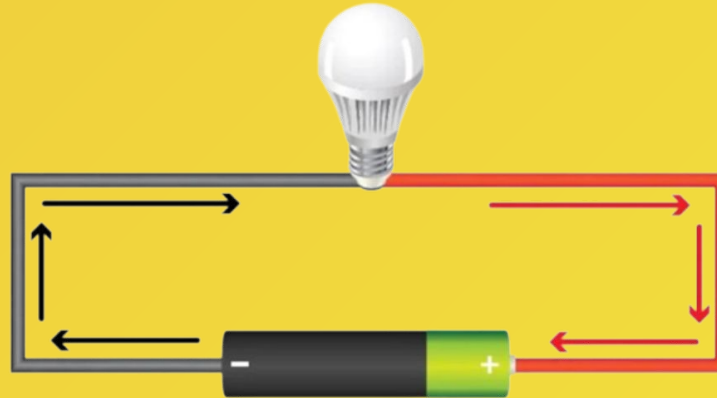
# What is a circuit?

A circuit is a closed loop that allows electric current to flow through it.

- Contains a **power source** that provides energy to the circuit
- Contains some way to turn the energy into **work**



In this simple circuit, the battery is the power source, and the light bulb converts electrical energy into light.



# Conductors and Insulators



Trying to move electricity through any material takes energy! However, it takes a lot more energy to move electricity through some materials compared to others.

It is very easy to move electricity through **conductors**.

It is very hard to move electricity through **insulators**.

Wires have a metal core because metal is a good conductor, so electricity moving through it won't lose much energy.

Wires have a plastic coating so that electricity won't move from the metal to you if you touch it. Plastic is a good insulator.

## 5 Electrical Conductors



silver



gold



copper



steel



sea water

## 5 Electrical Insulators



rubber



glass



oil



diamond




dry wood



# How does the switch work?



# How does the switch work?

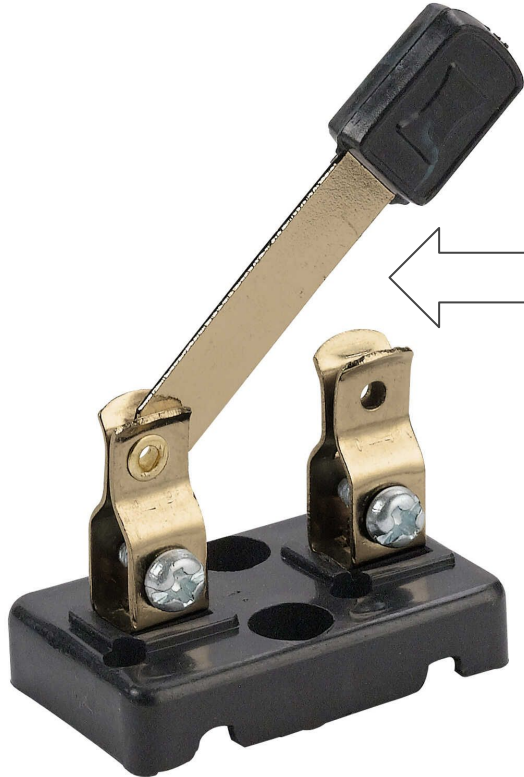


Right now, the electricity needs to go through the air (an insulator) to reach the other end of the switch.

Closing the switch would create a path made up of only conductors, so electricity can go through.

02



# Voltage, Current, & Resistance

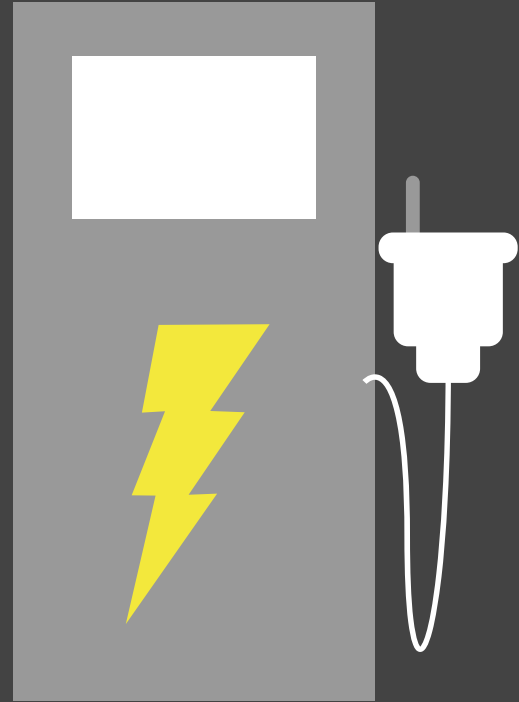
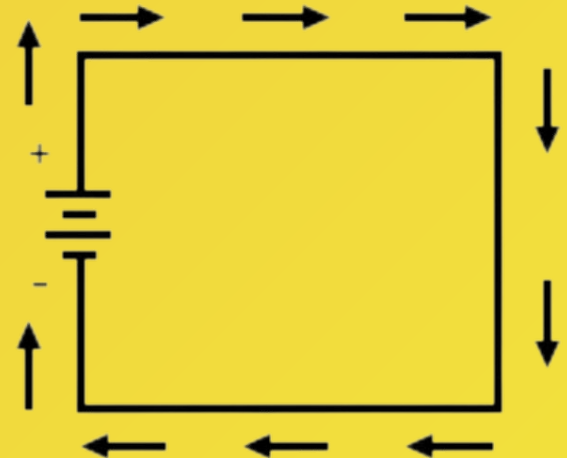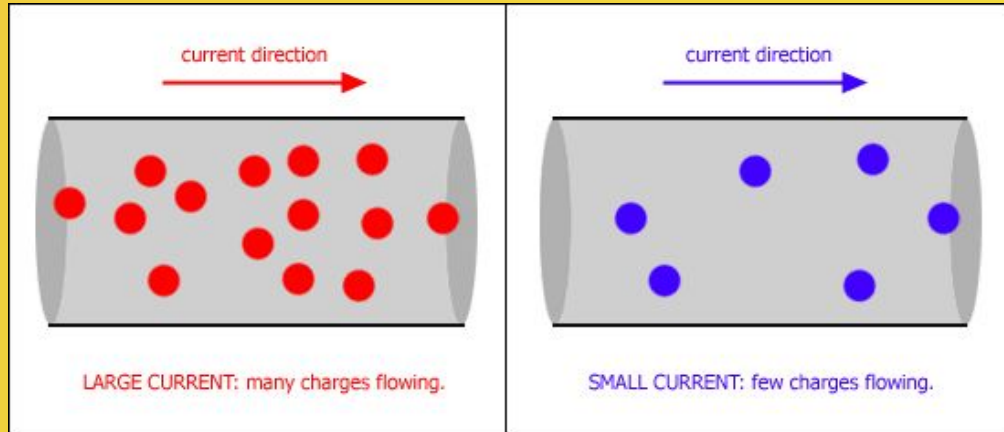
# Current

Current is the flow of charge.

- Specifically, it measures the **amount** of charge that flows through a point of a wire at a given time
- Measured in Amperes (A) → the higher the value, the higher the charge flow



# Voltage and Power


Voltage is a measure of the difference in energy between two points. **The higher the voltage drop, the more energy is used up between the two points.**

**Power = Voltage x Current**

The higher the current, the more charge is flowing every second.

The higher the voltage, the more energy is used up for every unit of charge.

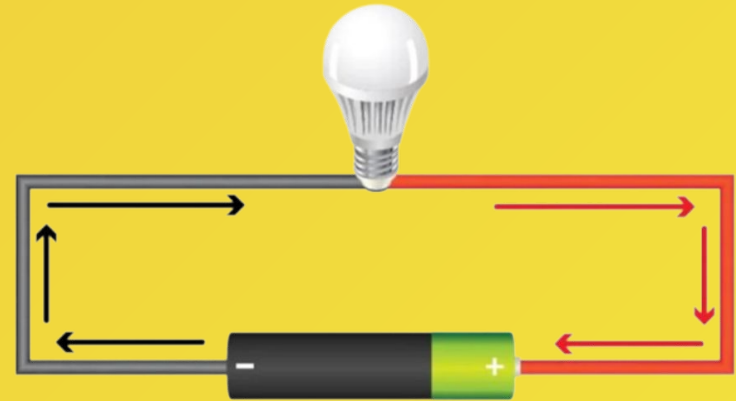With a high voltage and current, a circuit can expend energy very quickly. This means that the circuit has a high power.




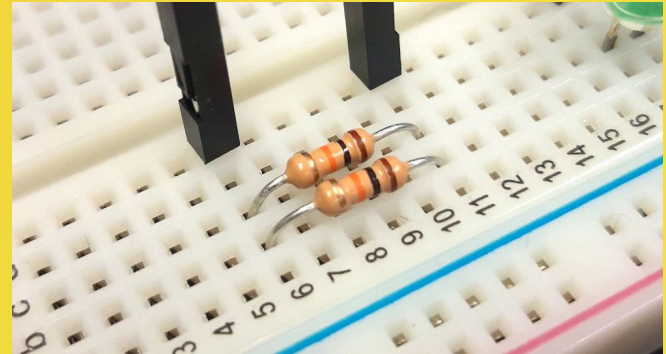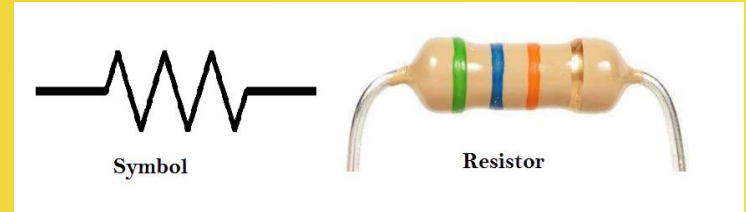
# Resistance



Resistance is the opposition to the flow of current.


- **A resistor limits the current going through the circuit by dissipating energy.**
- It takes energy to move electricity through a resistor! This means that there is a voltage drop.
- However, resistors are not perfect insulators.
- Measured in Ohms ( $\Omega$ )
- Different resistors have different resistances.
  - Higher resistance  $\rightarrow$  less current
- Think of a resistor as creating “traffic” for electrons
  - Reducing number of “lanes” prevents electrons from flowing through
- Lightbulbs can act as resistors!


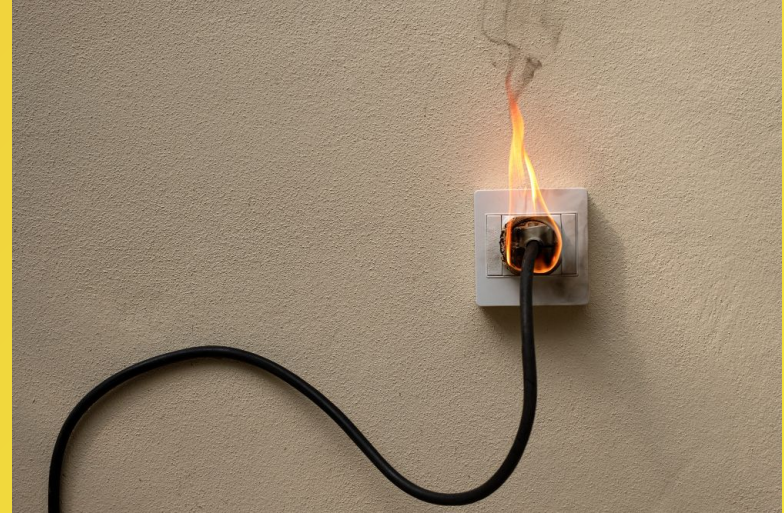
# Short Circuits




- Happens where there is too little resistance in the circuit
- All of the current flows from the positive to the negative end of the battery
  - The negative terminal is not designed to handle that current flow
  - This causes 🔥🔥🔥! Too much power!
- **Always make sure your circuit has a sufficient resistor or insulating component**
- **Never touch 2 electrodes together**






# Is this a short circuit?

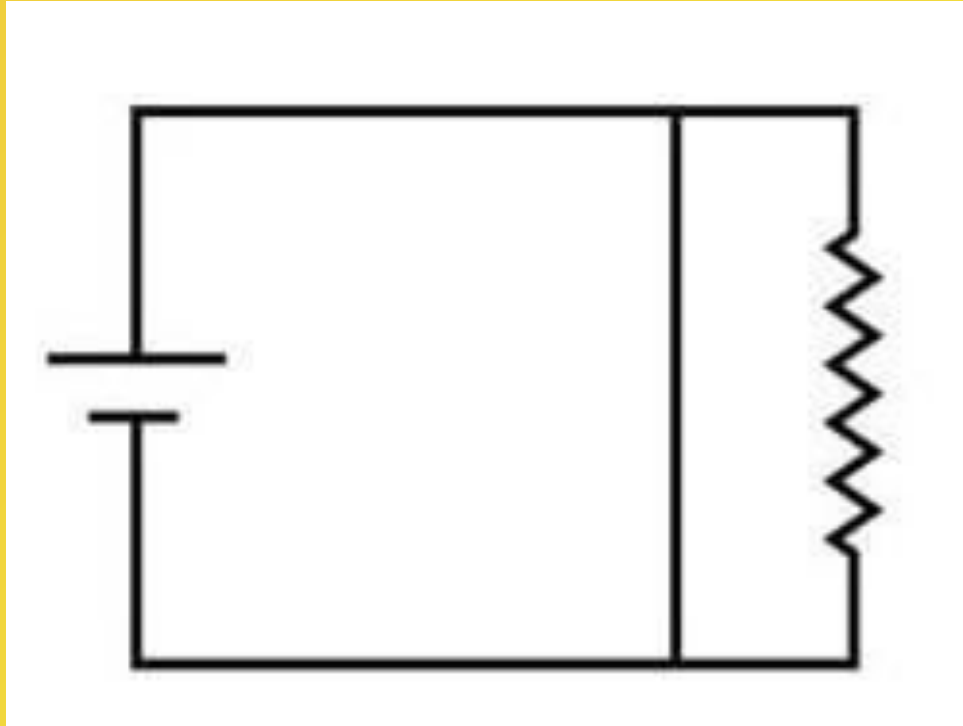



# Yes.

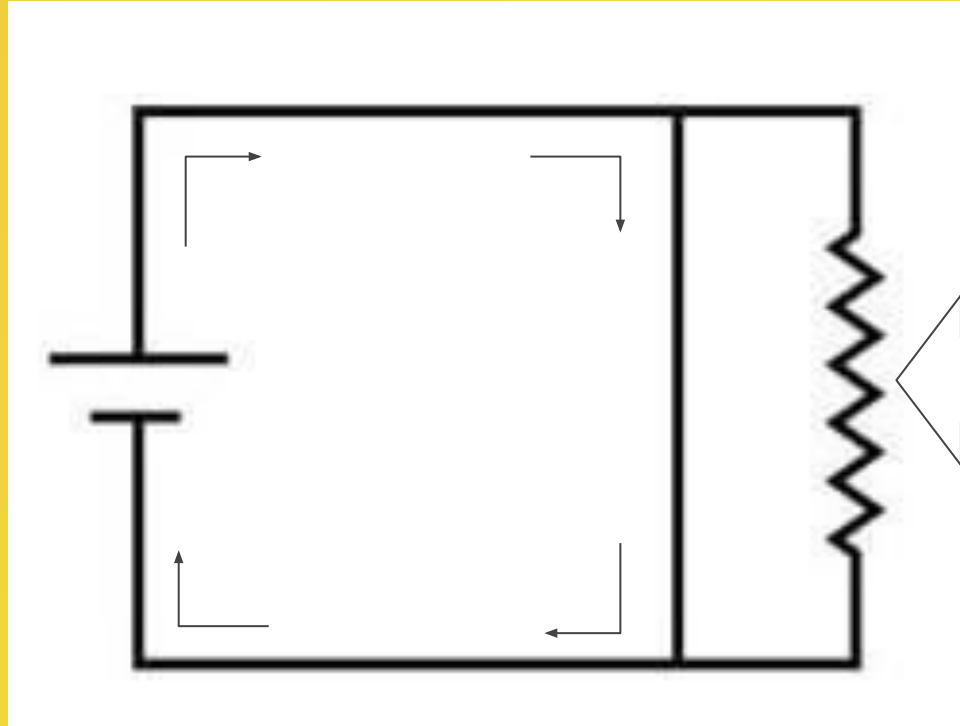

None of the current flows through the resistor because it's much easier to go through the wire!





03

# Series vs. Parallel




# Series



With elements in series, electricity has **ONE** path to go through the circuit.

Current has to go through ALL resistors.

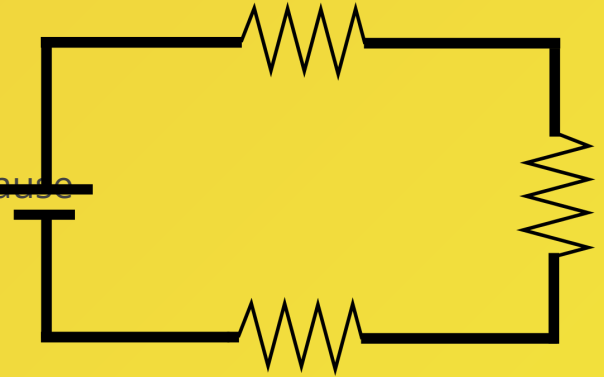- Equivalent resistance **increases** with more resistors, because it has to go through all of them.
  - $R_{eq} = R_1 + R_2 + R_3$
- Current is **the same** across all the resistors
  - Only one path to go
- Voltage is **divided** among the resistors
  - Ex. if 9 V battery and 3 resistors (of the same resistance), **3 V each**




# Parallel



With elements in series, electricity has **MULTIPLE** paths to go through the circuit.

Current only goes through ONE resistor. The most current will flow through the one with the **LEAST** resistance.

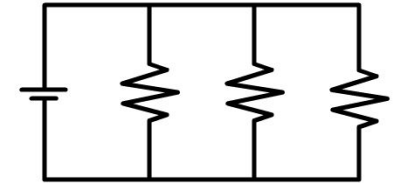- Equivalent resistance **decreases** with more resistors, because it can split up and go through any of them.
  - $R_{eq} = 1 \div (R_1 + R_2 + R_3)$
- Current **can be different** across all the resistors
  - The charges split up and move across all 3 branches
- Voltage is **the same** among the resistors
  - The difference in energy between the start and the end is the same





**Parallel Circuit**





# SERIES vs PARALLEL CIRCUITS

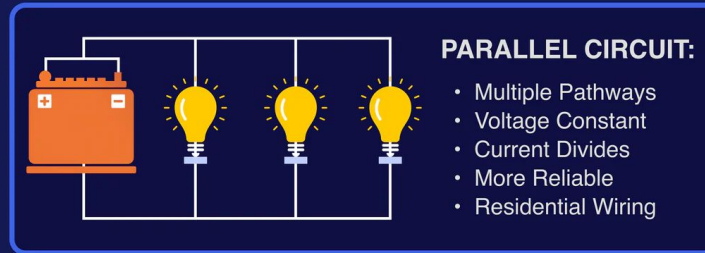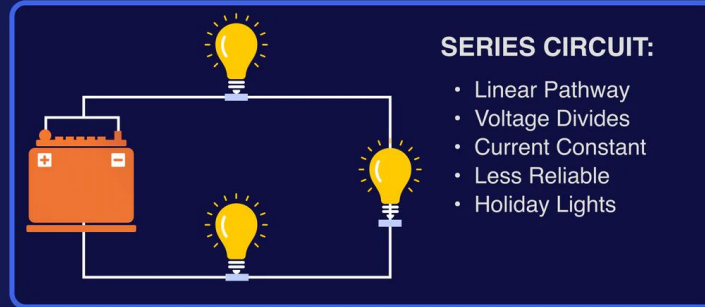

**NNC**




# Ohm's Law

$$V = IR$$


More voltage and less resistance will increase current.

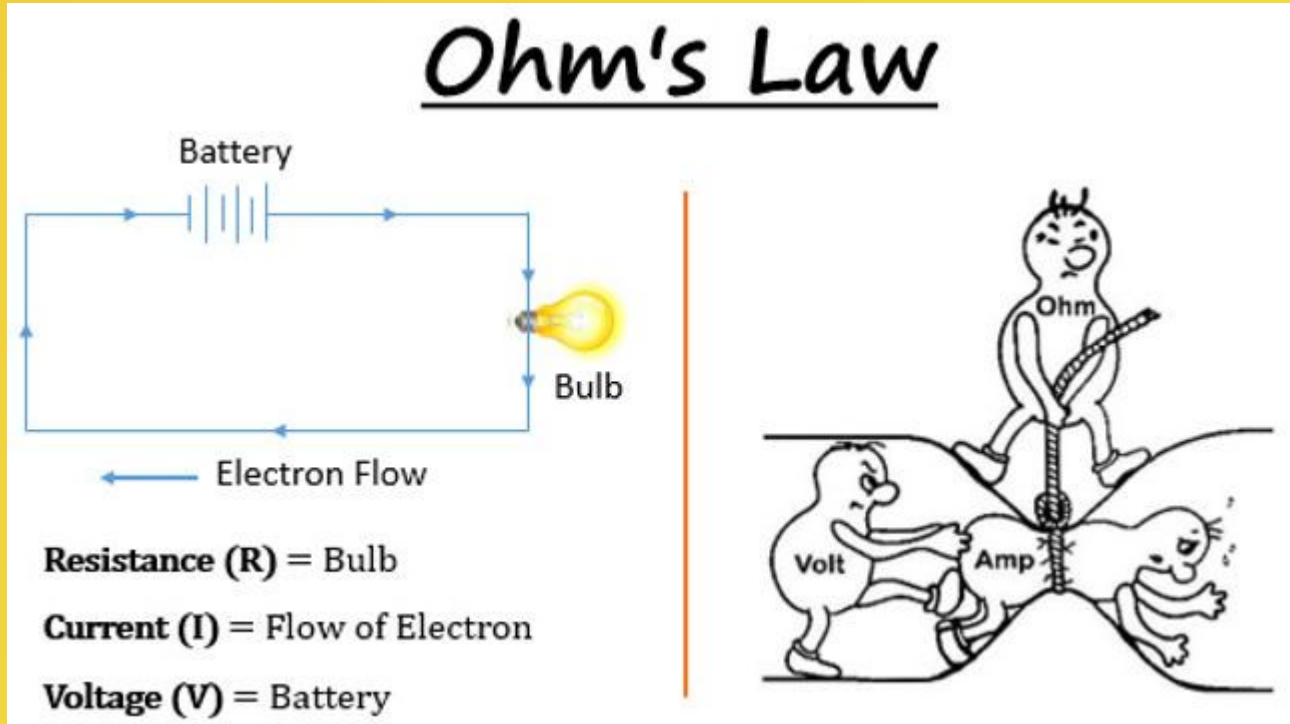More resistance and less voltage will decrease current.






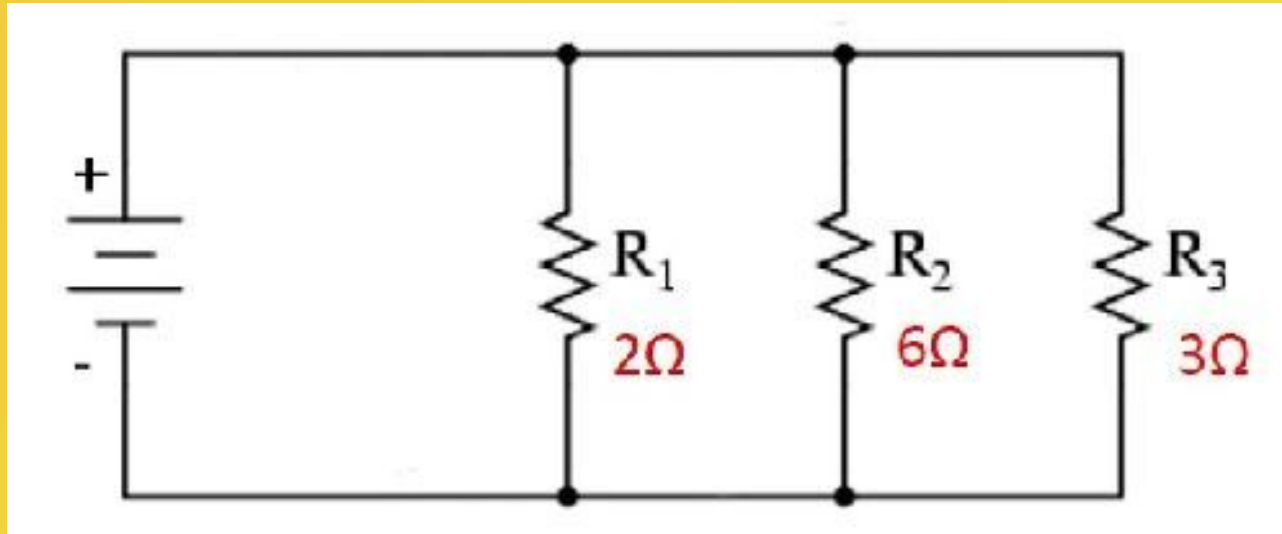**Which resistor has the most current going through it?**



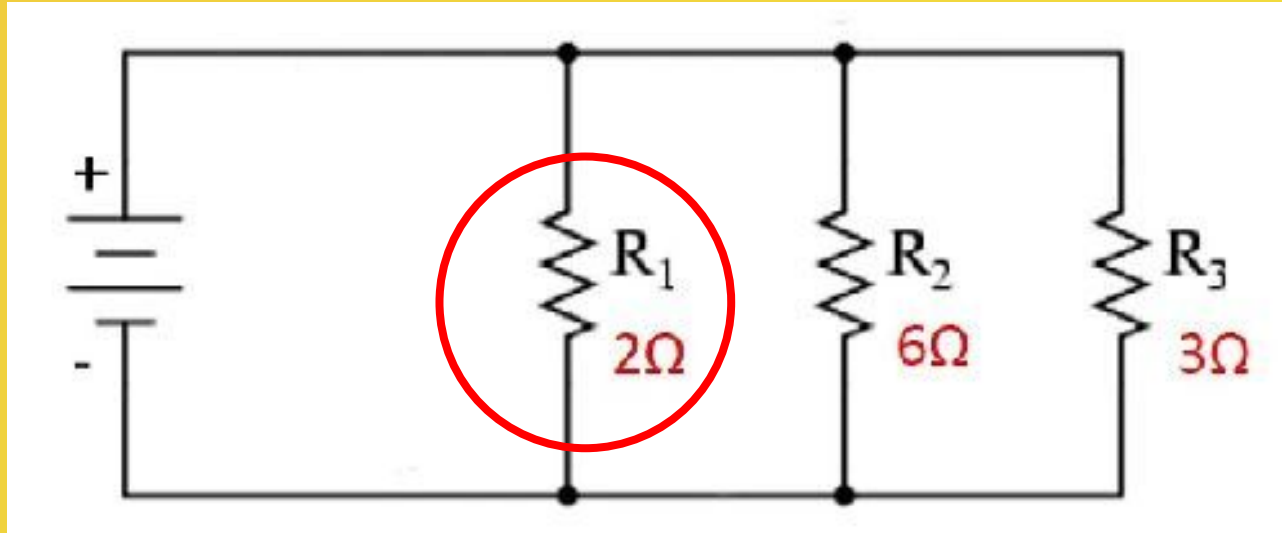
Which resistor has the most current going through it?




The voltage is the same for all three resistors, so the current must be highest in the resistor with the lowest resistance.



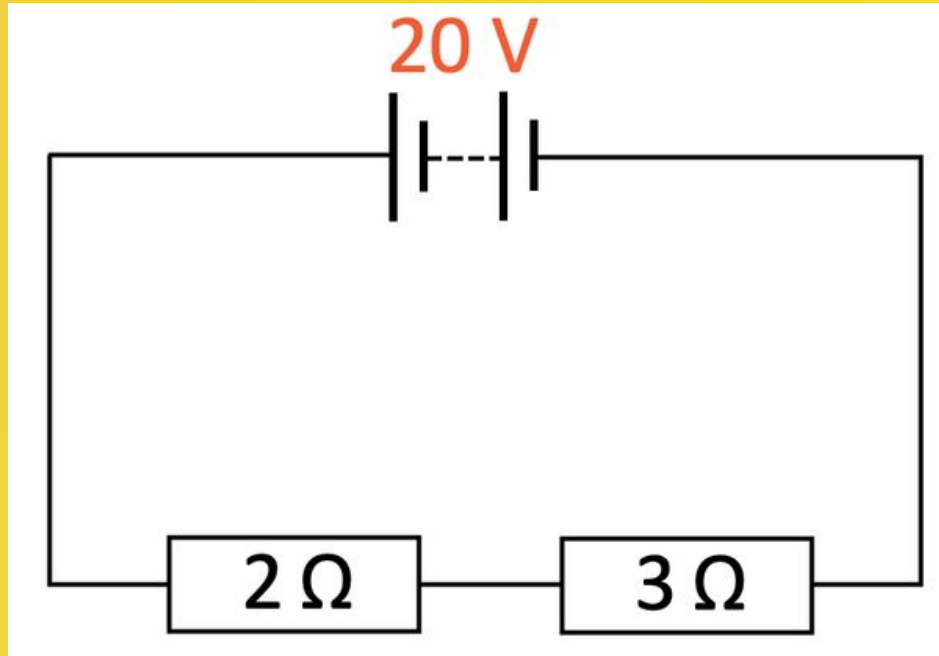**Which resistor has a greater drop in voltage across it?**




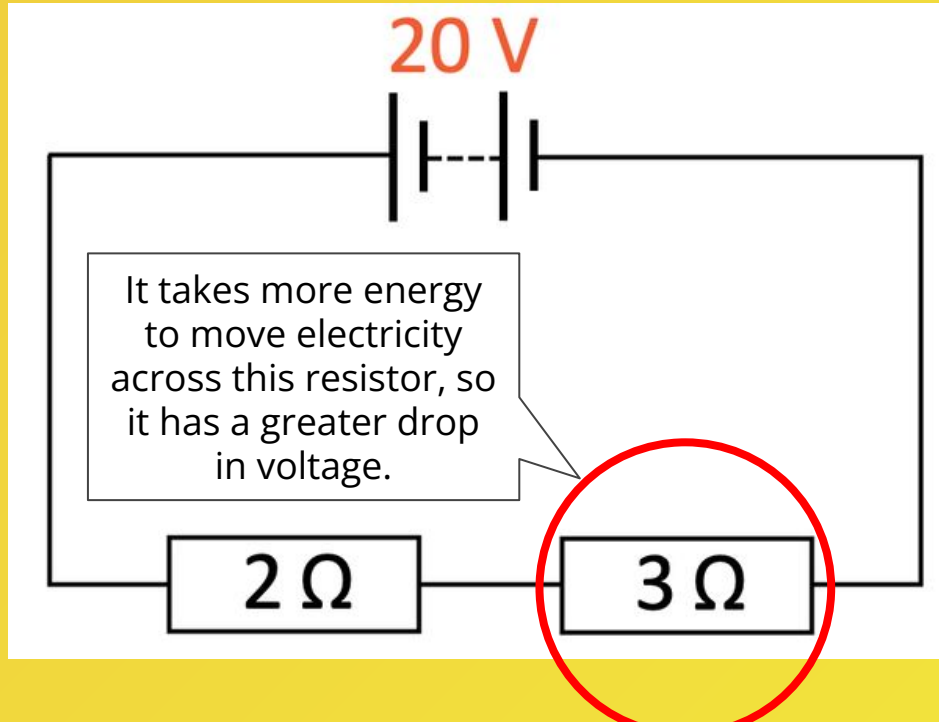**+ Which resistor has a greater drop in voltage across it?**



04

# Lightbulbs

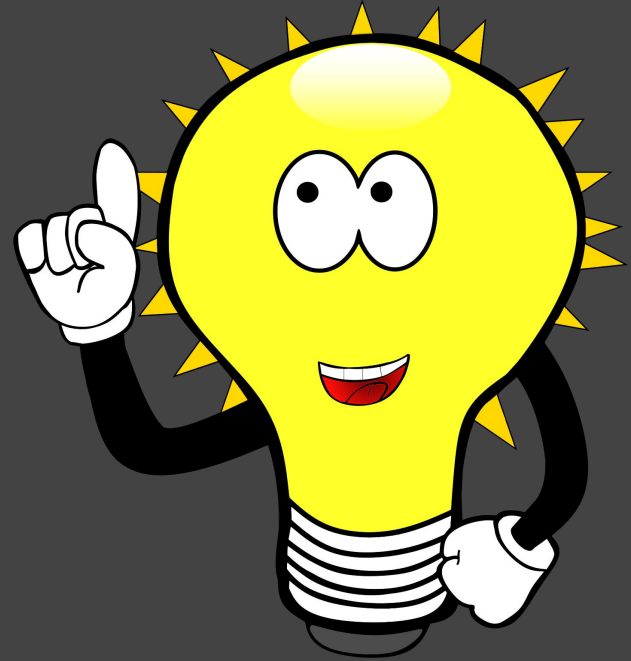

# Types of Lightbulbs



**Incandescent lightbulbs** work by having a thin filament in the middle that becomes so hot it starts glowing. Electricity can flow through it either way.



**LEDs** work by having electrons move from a high-energy region to a low-energy region in such a way that it releases light.

Electricity can only flow through it one way (long leg is positive).



They tend to have super low resistances, so make sure to add a resistor to avoid a short circuit.

# Lightbulbs



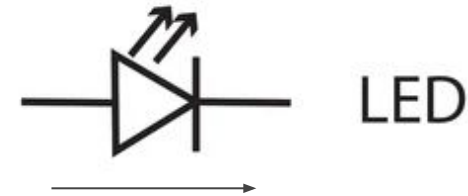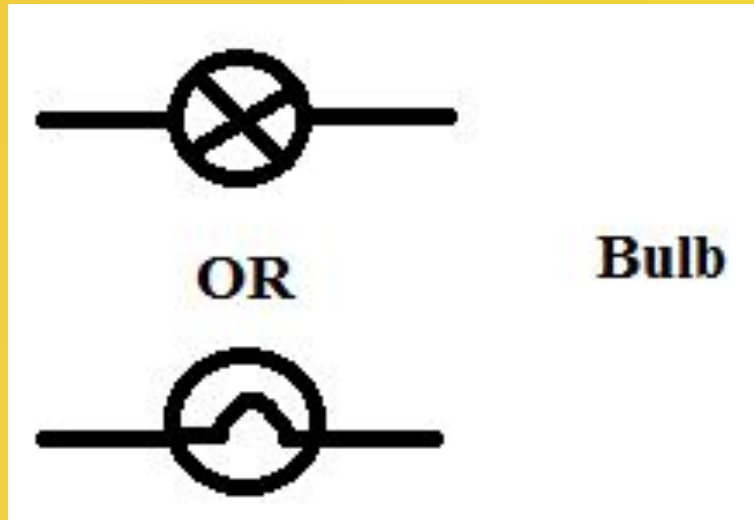**Lightbulbs will light when current passes through them.**

The higher the current, the brighter the bulb!




Electricity will only  
go this way.

shutterstock.com · 2211273453





# Can electricity flow this way?

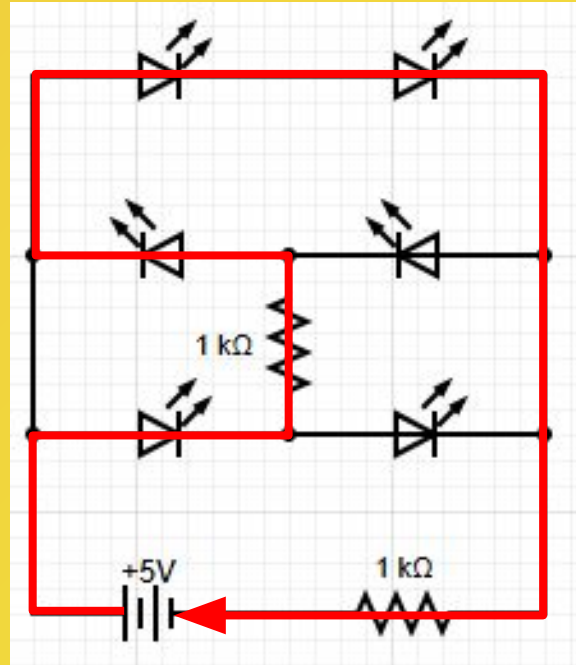



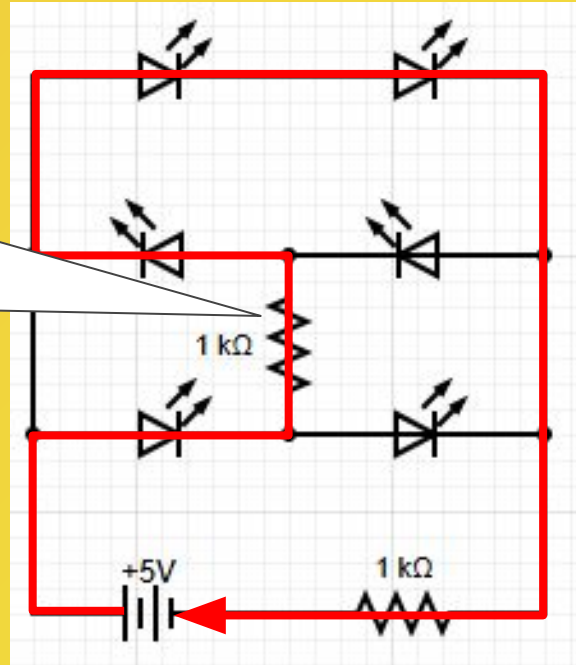
# No.



If the electricity went through the resistor, it would lose potential energy. It would not flow back to a wire that has a high potential energy.





# CRACK THE CIRCUIT





# Mystery Circuit!



+ + +

+ + + Try to draw up a diagram for how the switchboard in front  
+ + + of you is wired up!

+ + + Pro Tip: be deliberate and discuss every step

+ + +

+ + +

